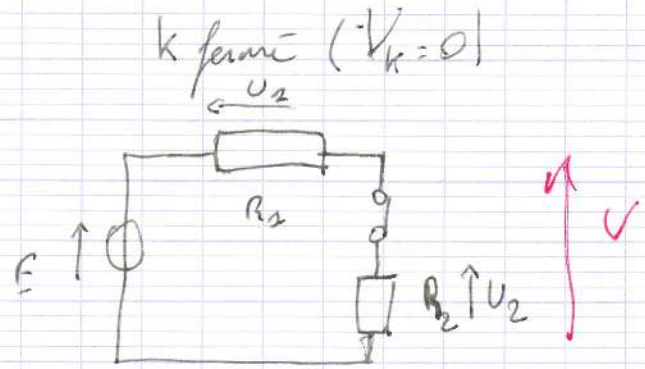


$$I = 0 \text{ A}$$


$$U_1 = U_2 = 0$$

$$V = E$$



$$V = U_2 = \frac{E \times R_2}{R_1 + R_2}$$

$$U_1 = \frac{E \times R_1}{R_1 + R_2}$$

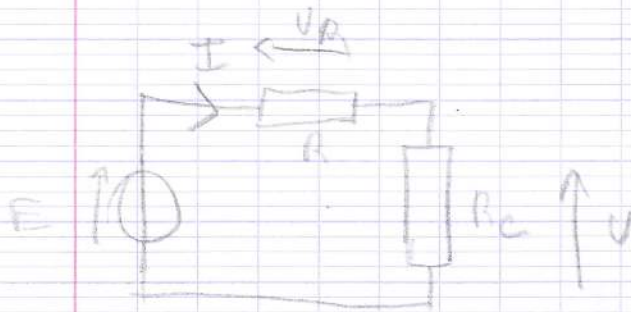

$$U_R = R \times I$$

$$V = R_c \times I \Rightarrow I = \frac{V}{R_c}$$

$$E - U_R - V = 0$$

$$E - R \times I - R_c \times I = 0$$

$$V = \frac{E \times R_c}{R + R_c}$$


$$I = \frac{V}{R_c} = \frac{20}{R_c}$$

$$V = U + U_R \Rightarrow R_c \times I + U \times R_c$$

$$V = (R + R_c) I \Rightarrow I = \frac{V}{R + R_c}$$


Kouvert
 $U_1 = U_2 = 0$ $V = E$

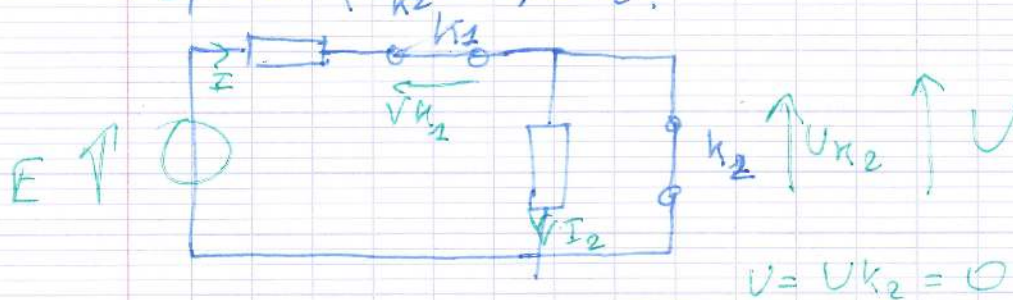K_1 fermé: $(V_{K_1} = 0) I_{K_2}$?
 K_2 fermé: $(V_{K_2} = 0) I_{K_2}$?



$V = U_{K_2} = 0$

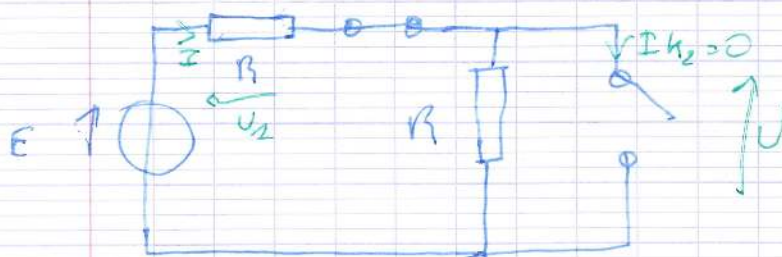K_1 fermé: $(V_{K_2} = 0) I_{K_2}$?
 K_2 fermé ouvert: $(I_{K_2} = 0) U_{K_2}$?



$U_1 = R \cdot I$
 $U = E - R \cdot I$
 $I = \frac{U}{R}$
 $U = \frac{1}{2} E$

$U = \frac{E \cdot R}{R + R} = \frac{E}{2}$

$$\frac{1}{4R} + \frac{1}{4R} = \frac{2}{4R} = \frac{1}{2R} = 2R + 2R = 4R \Rightarrow 2R_1 + R_2 = 3R_2$$


$$\frac{1}{6R} + \frac{1}{10R} = \frac{1}{10R} \Leftrightarrow 10R_1 + R_2 = 11R$$

$$\frac{1}{2R} + \frac{1}{2R} = R + R = \frac{1}{2R} + \frac{1}{2R} = R$$

$$\frac{1}{3R} + \frac{1}{2R} = 5R + R = \frac{1}{6R} + \frac{1}{6R} = \frac{7}{6R} = \frac{6R}{7}$$

$$\frac{1}{4R} + \frac{1}{4R} = 2R + 4R = \frac{1}{6R} + \frac{3}{2R} = \frac{4}{6R} + \frac{3}{6R} = 2R$$
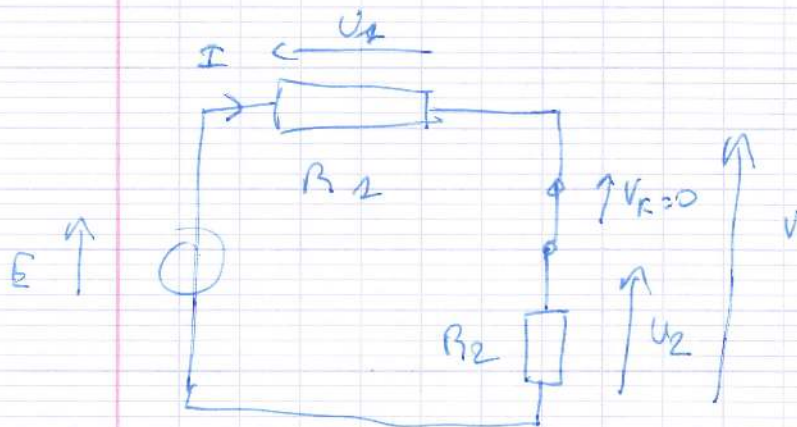
$$\frac{1}{2R} + \frac{1}{2R} = R + 2R = \frac{1}{3R} + \frac{1}{3R} = \frac{2}{3R} = \frac{3R}{2} + \frac{4R}{2} = \frac{7R}{2}$$



$$E - U_1 - U_2 = 0$$

$$V = U_2 + V_R$$

$$R_1 = \frac{U_1}{I}$$

$$R_2 = \frac{U_2}{I}$$

$$\boxed{E - U_1 - U_2 = 0}$$

$$E - U_2 - V = 0 \text{ with } V_R = 0$$


$$E - 3R_2 - R_2 = 0$$

$$E - 4R_2$$

$$V = U_2 = \frac{E \times R_2}{R_1 + R_2}$$

$$U_2 = E \times \frac{R_2}{R_2 + 3R_2} = E \times \frac{R_2}{4R_2} = \frac{E}{4} = \frac{10}{4} = 2,5 \text{ V}$$

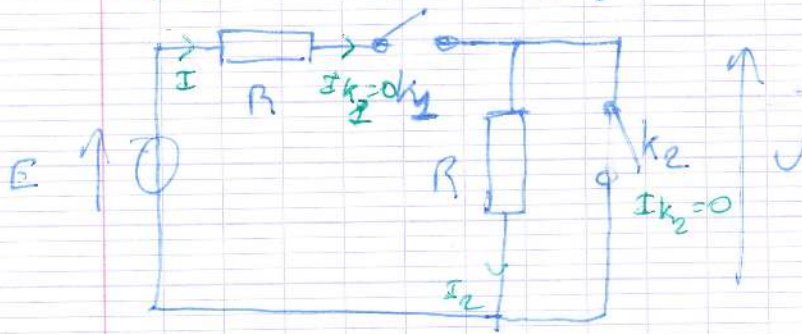
k_1 ouvert ($I_{k_2} = 0$) V_{k_2} ?
 k_2 ouvert ($I_{k_2} = 0$) V_{k_2} ?



$$I_2 = 0$$

$$U = R \cdot I_2 = 0$$

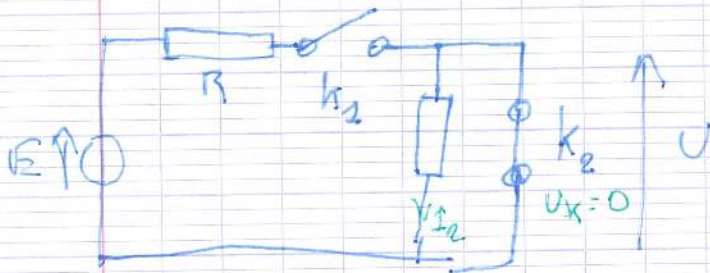k_1 ouvert ($I_{k_2} = 0$) V_{k_2} ?
 k_2 fermé ($V_{k_2} = 0$) I_{k_2} ?




$$I_2 = 0$$

$$U_k = R \cdot I_2 = 0$$

$$U = U_{k_2} = 0$$

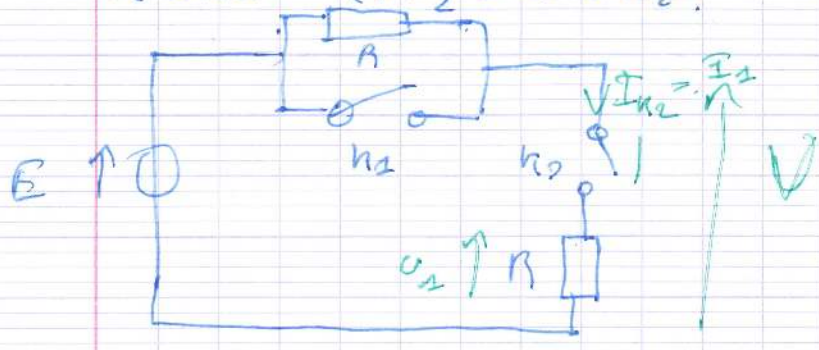
k_2 ouvert ($I_{k_2} = 0$) U_{k_2} ?
 k_2 ouvert ($I_{k_2} = 0$) U_{k_2} ?



$$I_1 = 0$$

$$U_2 = R_0 \cdot I_1 = 0$$

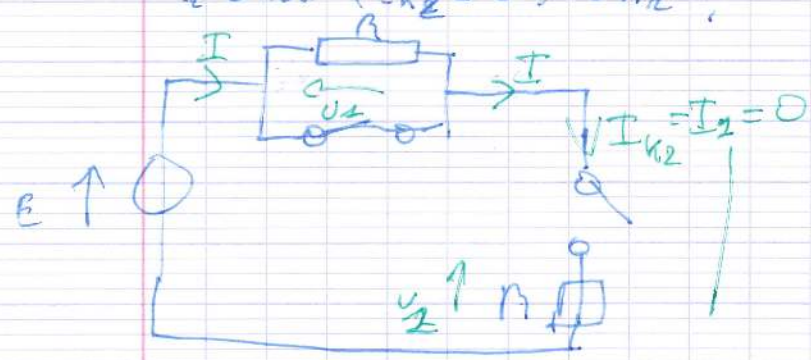k_2 fermé ($I_{k_2} = 0$) I_{k_2} ?
 k_2 ouvert ($I_{k_2} = 0$) U_{k_2} ?




$$I_{k_2} = 0 = I$$

$$U_2 = R_0 \cdot I_{k_2} = 0$$

$$E - U_2 - U = 0$$

$$E = U$$

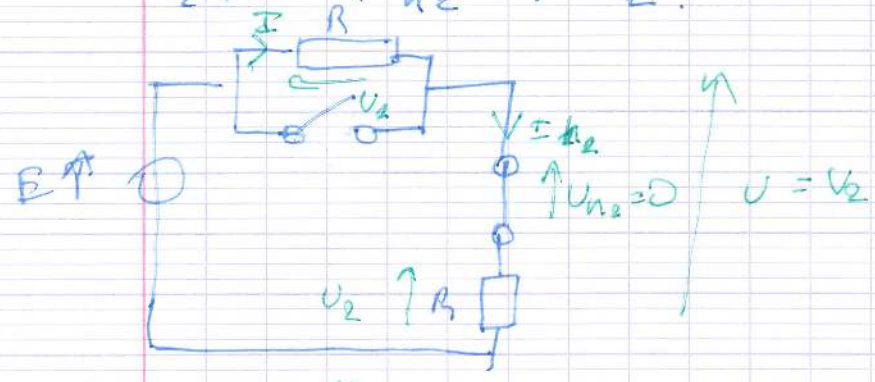
k_2 ouvert ($I_{k_2} = 0$) U_{k_2} ?
 k_2 fermé ($U_{k_2} = 0$) I_{k_2} ?



$$E - U_1 - U_2 = 0$$

$$U_2 = R_0 \cdot I$$

$$U_2 = R_0 \cdot I_{k_2}$$

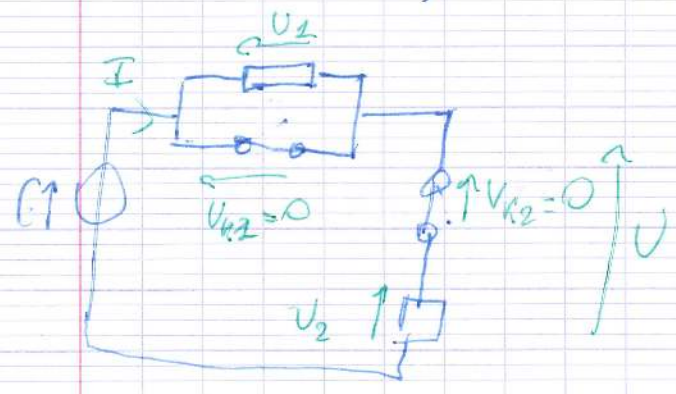


$$U_1 = 0$$

$$U = U_2$$

$$E - U_1 - U = 0$$

$$E = U$$

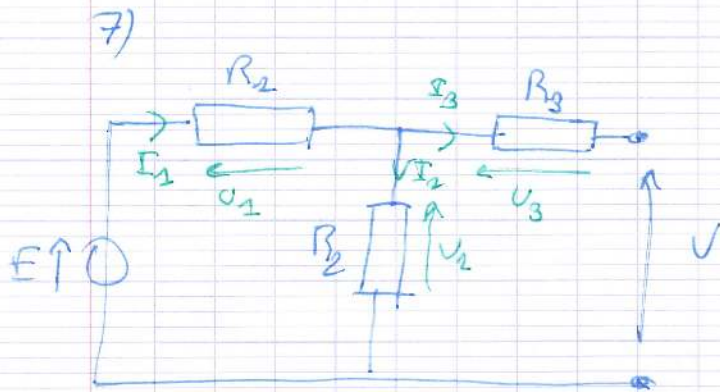

$$E - U_1 - U_3 - U = 0$$

$$U_2 =$$

$$E - U_1 - U_2 = 0$$

~~$$E - U_2 - U_3 - U = E - U_1 - U_2$$~~

$$U + U_3 - U_2 = 0$$

Or

$$U_1 = R_1 \cdot I_1$$

$$I_3 = 0$$

$$U_2 = R_2 \cdot I_2$$

$$I_1 = I_2 = I$$

$$U_3 = R_3 \cdot I_3$$

$$U_1 = R_1 \cdot I$$

$$U_2 = R_2 \cdot I$$

$$U_3 = 0$$

$$U = U_2$$


↓

Pot divider

$$U = \frac{E \cdot R_2}{R_1 + R_2} = \frac{10V \cdot 8k}{2k + 8k} =$$

Elatro
4/110

2

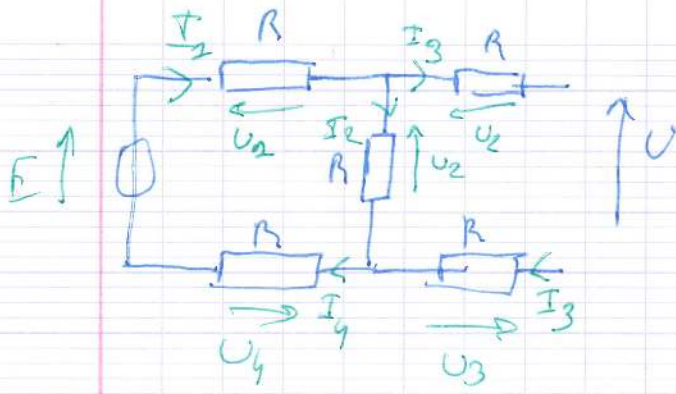

$$U = E \times \frac{R}{R_1 + R_2 + R_3}$$

$$E - U_1 - U_3 - U_{32} - U_4 = 0$$

$$E - U_1 - U_2 - U_4 = 0$$


$$I_3 = 0$$

$$U_2 = R_2 \cdot I$$

$$U_2 = R_2 \cdot I_2$$

$$U_{32} = U_3 - U_2$$

Exercice n°2:

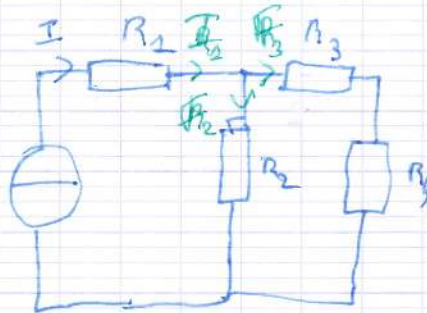

$$\frac{1}{R_3 + R_4} + \frac{1}{R_2}$$

$$\frac{1}{100 + 300} + \frac{1}{900} = \frac{3}{400} = \frac{400}{3}$$

$$+ 100 \Omega = \frac{700 \Omega}{3}$$

$$U_2 = R_2 \cdot I$$

$$I = I_2 + I_3$$

$$I_2 = \frac{U_{AB}}{R_2}$$

$$U_{AB} = R_2 \cdot I_2$$

$$U_2 = 100 \text{ V}$$

$$U_{AB} = (R_3 + R_4) \cdot I_3$$

$$U_{AB} = R_{AB} \cdot I$$

$$I_2 = \frac{U_{AB}}{R_2} = \frac{1}{R_2} \times I \times \frac{1}{\frac{1}{R_2} + \frac{1}{R_3 + R_4}}$$

$$I_2 = I_x \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_3 + R_4}}$$

$$I_3 = I_x \frac{1}{R_3 + R_4} \frac{1}{\frac{1}{R_2} + \frac{1}{R_3 + R_4}}$$

$$U_0 = ?$$

loi de Ohm $U_0 = -R_1 \cdot I_0$

loi de Kirchhoff $U_0 + U_1 - E_2 = 0$

$$U_0 = E_2 - U_1 = E + R_1 \cdot I_0$$

$$I_2 = ?$$

$$U_2 = R_2 \cdot I_2$$


$$E_2 + U_0 - E_3 = 0$$

$$U_2 = E_3 - E_2$$

$$I_2 = \frac{E_3 - E_2}{R_2}$$

Exercice n°2

2)

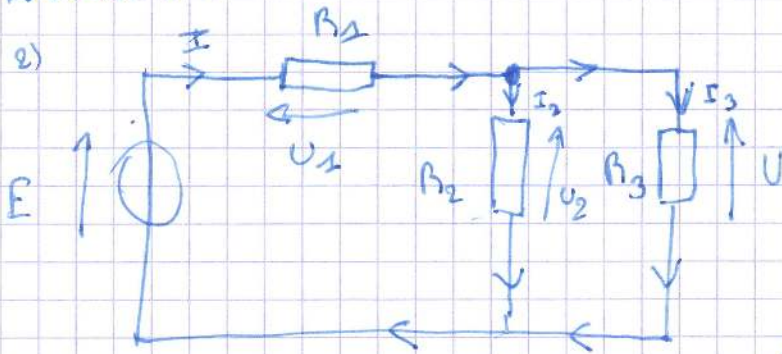

Loi des mailles:

$$\begin{cases} E - U_1 - U = 0 \\ E - U_2 - U = 0 \\ U - U_3 = 0 \end{cases} \quad U = (E - U_2)$$

Loi des nœuds:

$$\begin{cases} I = I_2 + I_3 \\ I = \frac{U_2}{R_2} + \frac{U_3}{R_3} \end{cases} \quad U_2 = U_3$$

$$E - R_1 \cdot I - R_2 \cdot I_2 = 0$$

$$R_1 \cdot I = R_2 \cdot I_2 - E$$

$$I = \frac{R_2 \cdot I_2 - E}{R_1} = \frac{R_2 \cdot \frac{U_2}{R_2} - E}{R_1} = \frac{U_2 - E}{R_1}$$

$$I = \frac{U}{R} = \frac{U_2}{R_2} + \frac{U_3}{R_3}$$

$$I_2 = \frac{U_2}{R_2} \quad I_3 = \frac{U_3}{R_3}$$

$$U = R \cdot I \quad E - U_2 - U_2 = 0$$

$$I_2 = I_3 = \frac{U}{R} = \frac{U}{R_2} + \frac{U}{R_3} = U \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$I_1 = (E - U_2) \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$I_1 = (E - R_1 \cdot I_1) \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$I_1 = E \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - R_1 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) I_1$$

Loi d'ohm

$$\begin{cases} U_1 = R_1 I_1 \\ U_2 = R_2 I_2 \\ U_3 = R_3 I_3 \end{cases}$$

Diviseur de tension

$$\frac{R_2 R_3}{R_2 + R_3}$$

$$R_2 + R_3$$

Diviseur de courant


$$\frac{R_2}{R_2 + R_3}$$

$$R_2 + R_3$$

$$R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$I_1 = \frac{E}{R_{eq}} = \frac{E}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$
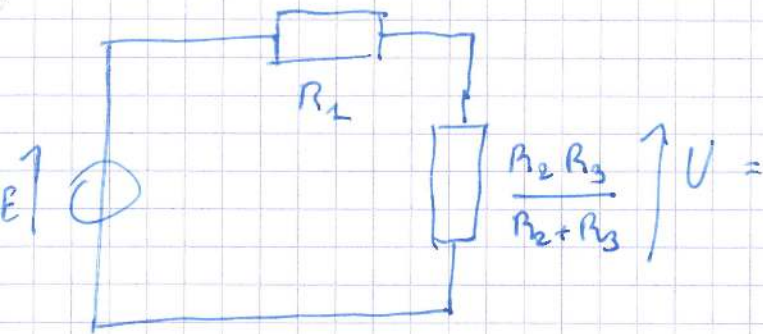
$$I_1 = \frac{60}{6,25 + \frac{10 \times 6}{10 + 6}} = \frac{60}{6,25 + \frac{60}{16}}$$



$$I_2 = \frac{U}{R_2} \quad I_3 = \frac{U}{R_3}$$

$$I_1 = I_2 + I_3$$

$$U = \frac{E \times \frac{R_2 R_3}{R_2 + R_3}}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

$$I_1 = E \cdot \frac{R_2 + R_3}{R_2 R_3} - R_1 \left(\frac{R_2 + R_3}{R_2 R_3} \right) I_1$$

$$I_1 \left(1 + \frac{R_1 (R_2 + R_3)}{R_2 R_3} \right) = E \cdot \frac{R_2 + R_3}{R_2 R_3}$$

$$I_1 \left(\frac{R_1 (R_2 + R_3) + R_2 R_3}{R_2 R_3} \right) = E \cdot \frac{R_2 + R_3}{R_2 R_3}$$

$$I_1 = \frac{E (R_2 + R_3)}{R_2 R_3 + R_1 (R_2 + R_3)}$$


$$R_2 I_2 = R_3 I_3 \quad I_3 = \frac{R_2}{R_3} I_2$$

$$I_2 = I_1 - I_3$$

$$I_2 = I_1 - \frac{R_2}{R_3} I_2$$


$$I_2 = \frac{R_3}{R_2 + R_3} I_1$$
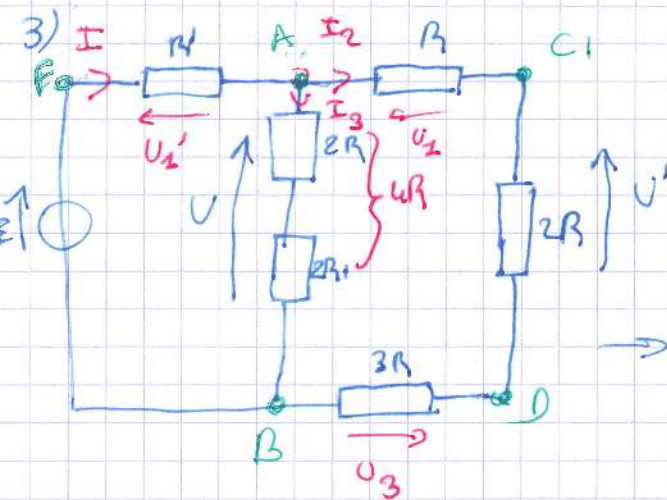
$$I_2 \left(1 + \frac{R_2}{R_3} \right) = I_1$$



$$I_2 = \frac{E \times R_3}{R_2 R_3 + R_1 (R_2 + R_3)}$$
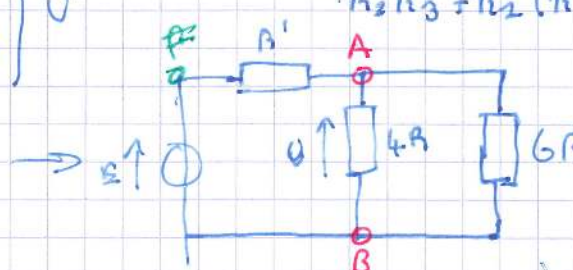
$$I_3 = \frac{E \times R_2}{R_2 R_3 + R_1 (R_2 + R_3)}$$




Lois des mailles

$$\begin{cases} E - U_1' - U = 0 \\ E - U_1' - U_1 - U' - U_3 = 0 \\ U - U_2 - U' - U_3 = 0 \end{cases}$$

Lois des nœuds
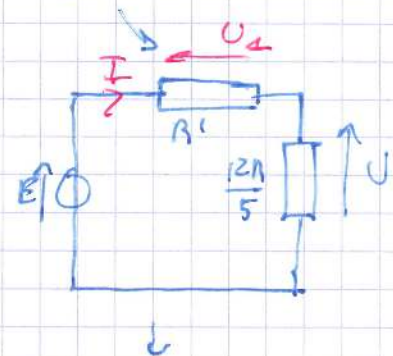
$$\begin{aligned} I &= I_2 + I_3 \\ I &= \frac{U_2}{R_2} + \frac{U_3}{R_3} \end{aligned}$$



$$U = \frac{E}{4} \quad U' = \frac{U \times 2R}{2R + R + 3R}$$

$$U' = \frac{U}{3} = \frac{E}{12}$$

$$E - U_1 - U = 0$$

$$U_2 = R_1 \cdot I$$

$$U = \frac{12R}{5} \cdot I$$


$$U = \frac{E \times \frac{12R}{5}}{R_1' + \frac{12R}{5}} = \frac{E \times 12R}{5R_1' + 12R} = \frac{E}{4}$$

$$48R = 12R + 5R_1'$$

$$R_1' = 36R/5$$


Division de tension :

Association en série de résistance

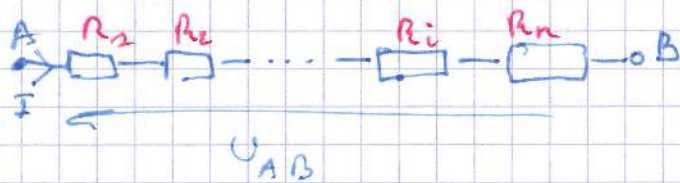


$$U_i = R_i \cdot I$$

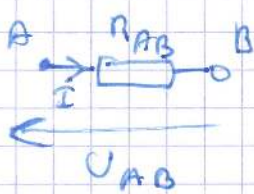
$$U_i = \frac{U_{AB} \cdot R_i}{\sum_k R_k}$$




$$R_{AB} = \sum_k R_k$$

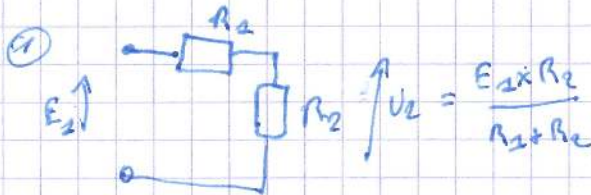
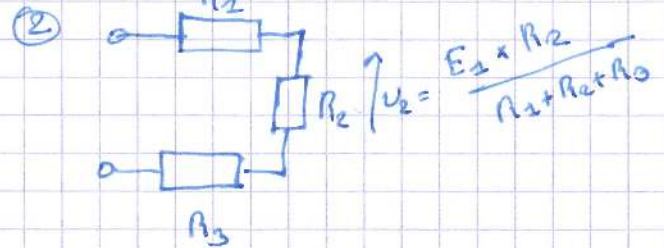
$$U_2 = \frac{E_1 \times R_2}{R_1 + R_2}$$



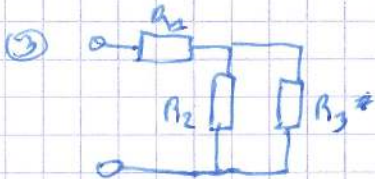
$$U_2 = \frac{E_1 \times R_2}{R_1 + R_2 + R_3}$$




Division de courant

Association de parallèle de résistance

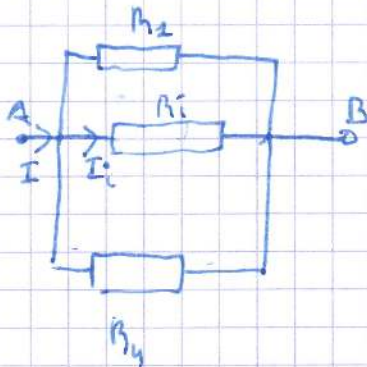

$$I_i = U_{AB} \cdot G_i$$

$$I_i = \frac{I \cdot G_i}{\sum_k G_k}$$

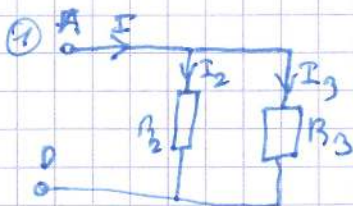


$$I_2 = \frac{I \times G_2}{G_2 + G_3} = \frac{I \times \frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{I \times R_3}{R_2 + R_3}$$

$$I_1 = \frac{I \times \frac{1}{3}R}{\frac{1}{3}R + \frac{1}{R}} = \frac{1}{4}I$$

Tension: → Loi d'Ohm

Courant → loi des Mailles

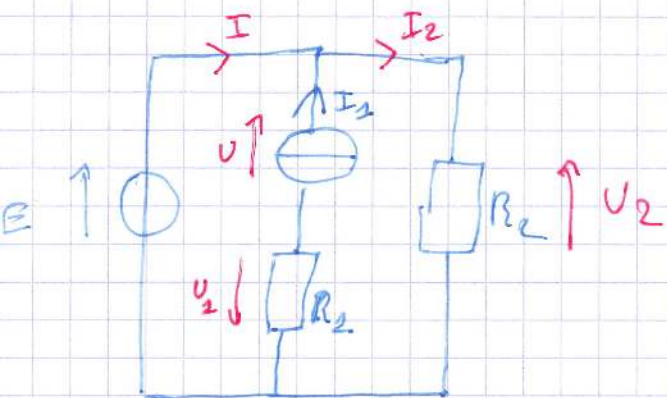

Loi des nœuds:

$$I_2 = I + I_1$$

Loi des mailles

$$E - U_2 = 0$$

$$E - U + U_2 = 0$$

Loi d'Ohm:


$$U_2 = R_2 \cdot I_1 \quad U_2 = R_2 \cdot I_2$$

$$\begin{cases} E = R_2 \cdot I_2 \\ E - U + R_2 \cdot I_1 = 0 \\ I_2 = I + I_1 \end{cases}$$

$$U = E + R_2 \cdot I_1$$

$$I = I_2 - I_1$$

$$I = \frac{E}{R_2} - I_1$$

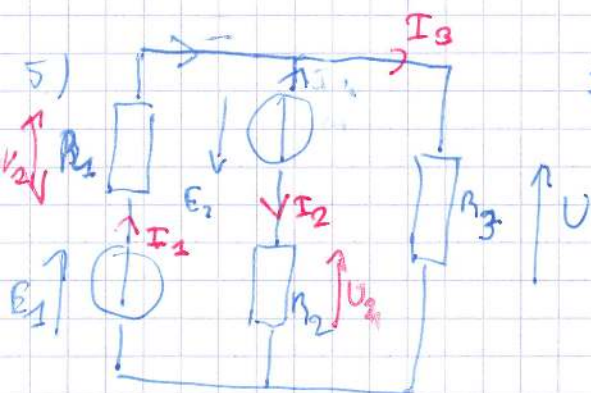

Loi des nœuds:

$$I_1 = I_2 + I_3$$

Loi des mailles

$$E_1 - U_2 - U = 0$$

$$E_1 - U_2 + E_2 - U_2 = 0$$

$$U_2 - E_2 - U = 0$$

Loi d'Ohm:

$$U = R_3 \cdot I_3$$

$$U_2 = R_2 \cdot I_2$$

$$U_2 = R_2 \cdot I_2$$

$$U = U_2 - E_2$$

$$\begin{cases} U = E_1 - U_2 \\ U_2 = R_2 \cdot I_2 \\ I_1 = I_2 + I_3 \end{cases}$$

$$\begin{cases} U = R_2 \cdot I_2 - E_2 \\ U = E_1 - R_2 \cdot I_2 \end{cases}$$