

$$E_2 - U_3 - U_1 - U_2 = 0$$


$$R_3 I + R_1 I + R_2 I = E_2$$

$$I = \frac{E_2}{R_1 + R_2 + R_3}$$



$$E_{th} - U_1 - U_2 = 0$$

$$\begin{aligned} E_{th} &= R_1 I + R_2 I \\ &= \frac{R_1 + R_2}{R_1 + R_2 + R_3} E_2 \end{aligned}$$


$R_{th}$

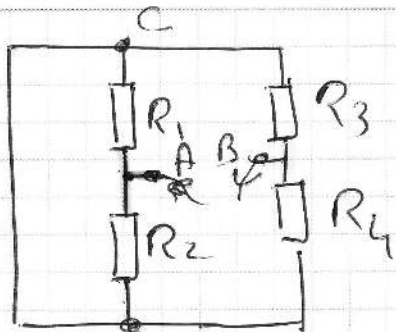

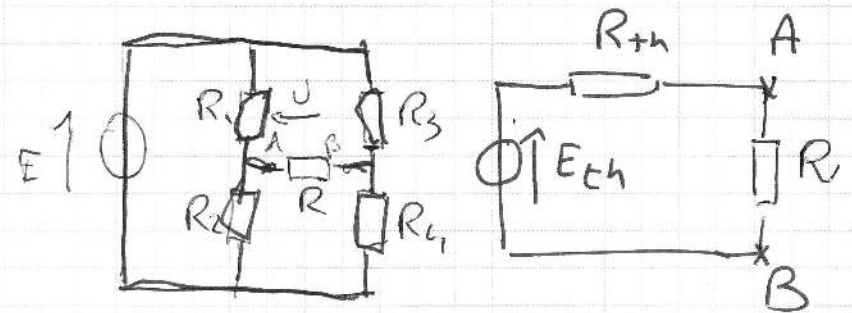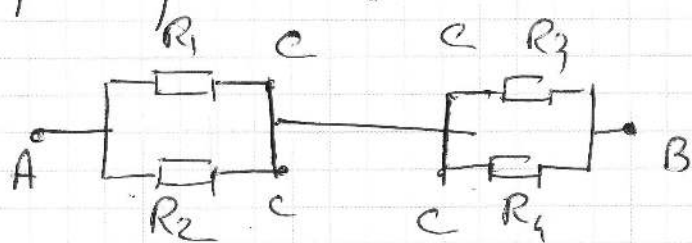$R_{eq}$  vue depuis A et B : On imagine que le courant arrive par A et repart par B.



$E_{th}$ :

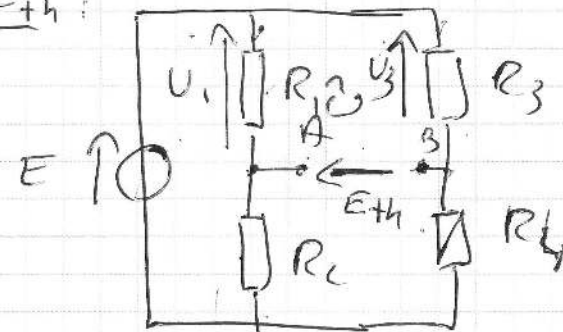

Circuit ouvert entre A et B

$\Rightarrow$  même courant de  $R_1$  et  $R_2$




même courant de  $R_3$  et  $R_4$

$$\Rightarrow R_1 \text{ et } R_2 \text{ en série} \Rightarrow U_1 = \frac{R_1}{R_1 + R_2} E$$

$$R_3 \text{ et } R_4 \text{ en série} \Rightarrow U_3 = \frac{R_3}{R_3 + R_4} E$$

Loi des mailles:  $U_1 - U_3 + E_{th} = 0$

$$E_{th} = U_3 - U_1$$

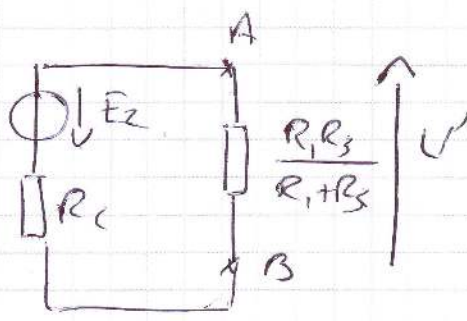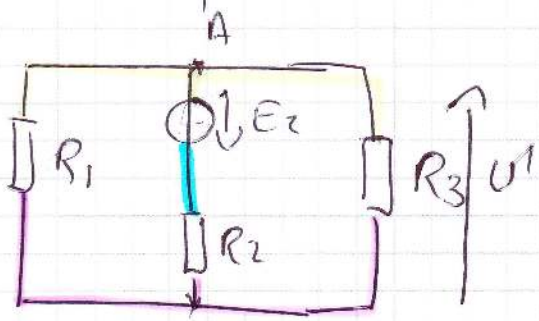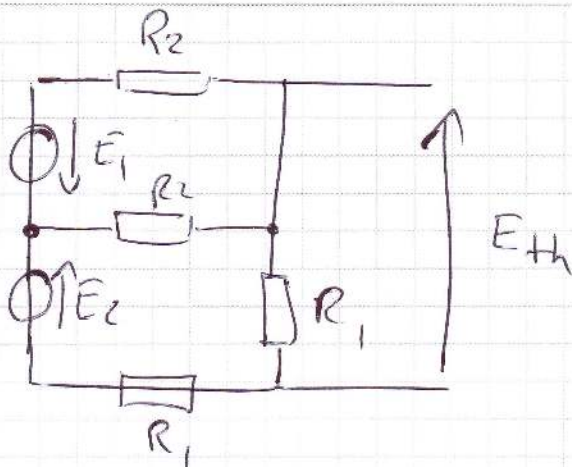

$$U' = \frac{\frac{R_1 R_3}{R_1 + R_3}}{\frac{R_1 R_3}{R_1 + R_3} + R_2} E_2$$