
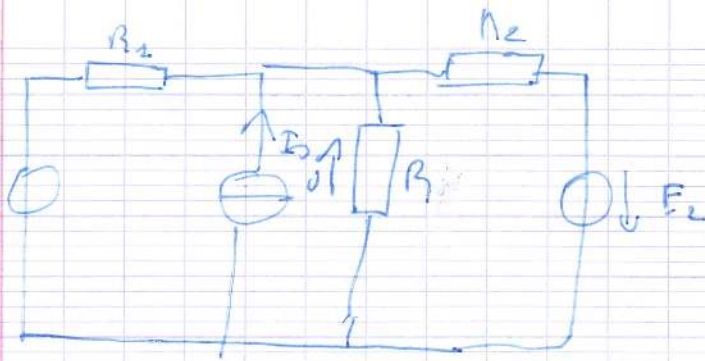


Electro
13/12

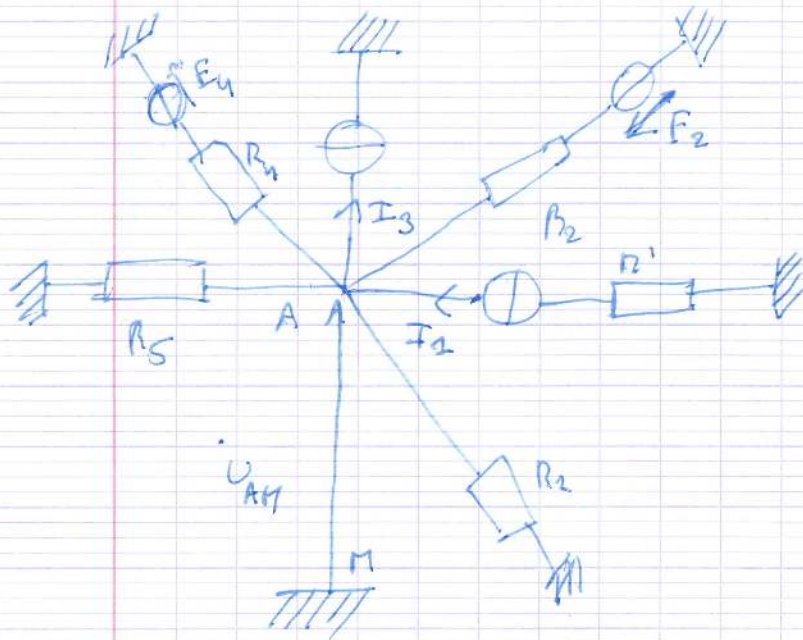


$$U = \frac{\frac{E_1}{R_1} + I_0 - \frac{E_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R} + \frac{1}{R_2}}$$

Théorème de Millman



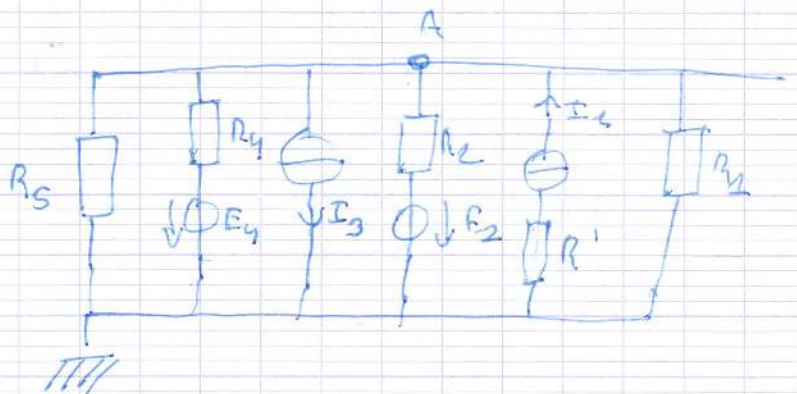
$$U = \frac{\sum_k \frac{E_k}{R_k} + \sum I_i}{\sum_k \frac{1}{R_k}}$$



E_1

Superposition


①

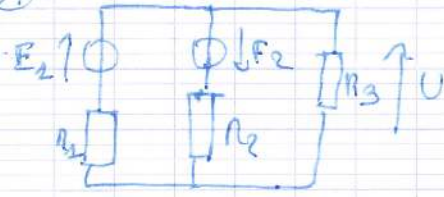

$$U_2 = \frac{\frac{E_1}{R_1} - \frac{E_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


$$U = \frac{E_1 R_2 R_3 - E_2 R_1 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2}$$

②

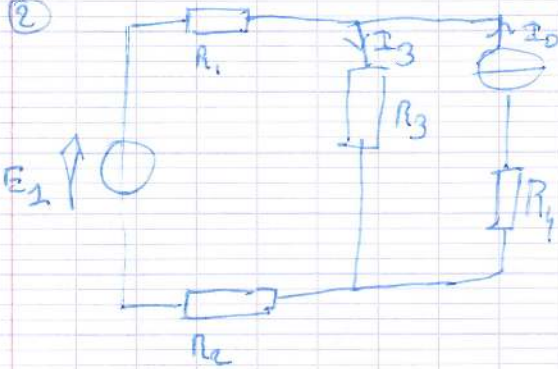


$$U_3 = \frac{\frac{E_1}{R_1 + R_2} + I_4}{\frac{1}{R_1 + R_2} + \frac{1}{R_3}}$$

E_2 :

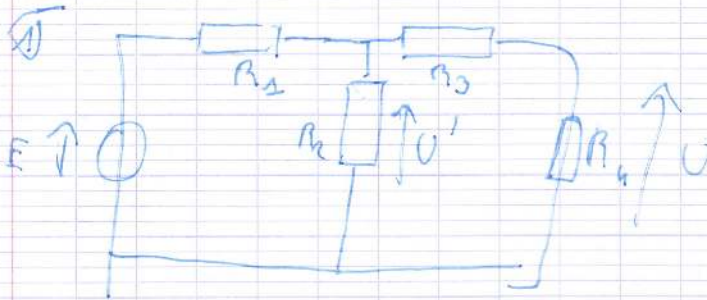

$$U' \times \frac{R_3 R_4}{R_3 + R_4}$$
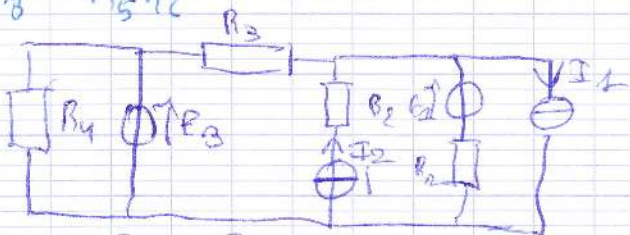
$$U' = \frac{\frac{E_1}{R_1 + R_2} + \frac{E_2}{R_3}}{\frac{1}{R_1 + R_2} + \frac{1}{R_3} + \frac{1}{R_3 + R_4}}$$



$$U = \frac{\frac{E_1}{R_3} + \frac{E_2}{R_2} + I_2 - I_4}{\frac{1}{R_3} + \frac{1}{R_4}}$$

α
 β
 $\gamma < \delta \Delta$
 ϵ
 ϕ

θ



$$\frac{E}{R_1 R_2}$$




$$\frac{1}{R_1 + R_2} +$$

$$\frac{3R}{3R+R}$$

$$U = \frac{E_1}{R} + \frac{E_2}{R} = \frac{E_1 + E_2}{\frac{3}{R}} = \frac{E_1 + E_2}{3}$$

10V
10mA

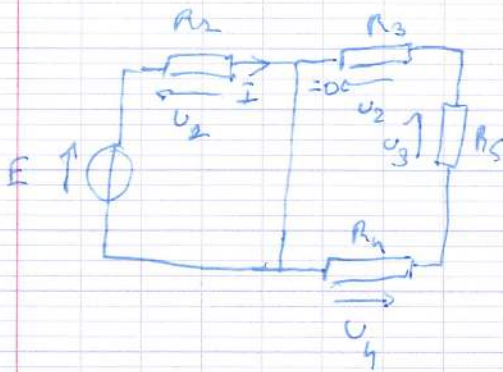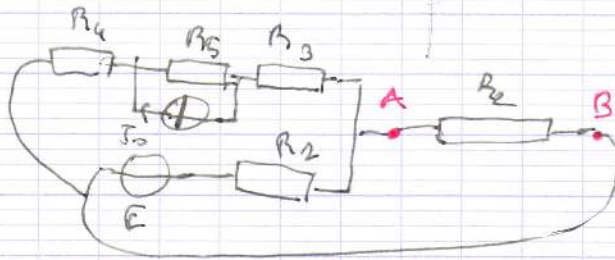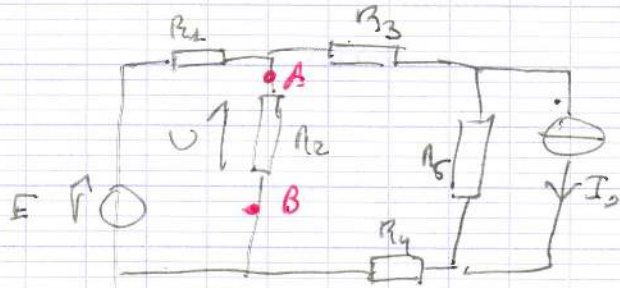- $R_1 = 3 \Omega$
- $R_2 = 1,2 k\Omega$
- $R_3 = 500 \Omega$
- $R_4 = 1,5 k\Omega$
- $R_5 = 2R$



$$E - U_2 = 0$$


$$U_2 = R_2 \times I_{cc}$$

$$E - R_2 I_{cc} = 0$$

$$I_{cc} = \frac{E}{R_2}$$


Norton

Caol:

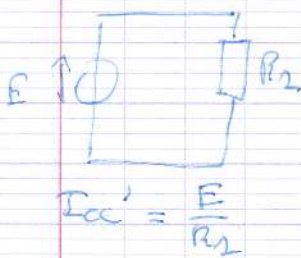

$$I_{cc}' = \frac{E}{R_1}$$

Caol:

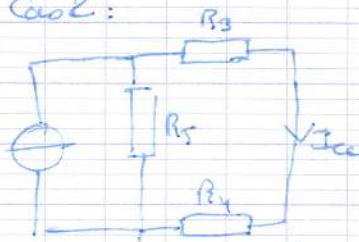


$$I_{cc}'' = -I_0 \times \frac{1}{\frac{1}{R_3 + R_4} + \frac{1}{R_5}}$$

$$I_{cc}'' = -I_0 \times \frac{1}{\frac{R_3 R_4}{R_3 + R_4} + R_5}$$

$$I_{cc}'' = -I_0 \times \frac{R_5}{R_3 + R_4 + R_5}$$

E2

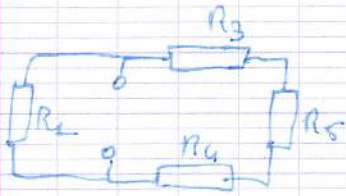

$$G_N = \frac{1}{R_3 + R_4 + R_5} + \frac{1}{R_2} = \frac{1}{R_N}$$

$$\frac{1}{R_N} = \frac{R_2 + R_3 + R_4 + R_5}{R_2(R_3 + R_4 + R_5)}$$

$$R_N = \frac{R_2(R_3 + R_4 + R_5)}{R_2 + R_3 + R_4 + R_5}$$

$$I_{a1} \frac{E}{R_2} - \frac{I_0 R_5}{R_3 + R_4 + R_5} = I_N = 5 \text{ mA}$$